

32733

(Pages : 3)

Name.....

Reg. No.....

**FIRST SEMESTER M.Sc. DEGREE (REGULAR/SUPPLEMENTARY)
EXAMINATION, NOVEMBER 2022**

(CBCSS)

Physics

PHY IC 04—ELECTRONICS

(2019 Admission onwards)

Time : Three Hours

Maximum : 30 Weightage

Section A*Answer all questions.**Each question carries weightage 1.*

1. What is unity-gain bandwidth of an operational amplifier ?
2. How can you change the frequency of emission in a LED ? Give any *two* examples for different colours.
3. Briefly explain radiative transition in a tunnel diode.
4. Write any *two* differences between common source and common drain operations of FET.
5. Briefly explain the advantages of Karnaugh map in logic circuit design.
6. Distinguish between microprocessor and Microcomputer.
7. Write a short note on population inversion.
8. How can you convert an SR Flip-flop to a JK Flip-flop ?

(8 × 1 = 8 weightage)

Section B*Answer any two questions.**Each question carries weightage 5.*

9. With the help of a logic diagram explain the working of a ring counter.
10. How can you construct an active low pass filter using operational amplifier ? Explain its working.

Turn over

11. Explain the different biasing techniques used in JFET and also explain the working of Source amplifier.
12. With the help of an R - 2R network circuit explain the conversion of a 4 bit digital signal.


(2 × 5 = 10)

Section C

Answer any **four** questions.


Each question carries weightage 3.

 13. Show how an asynchronous counter can be implemented having a modulus of 12 with binary sequence from 0000 through 1011.
14. For the JFET in the given figure, $V_{GS(off)}$ is -3 V and I_{DSS} is 10 mA . Determine the value of V_{DD} required to put the device in constant current area of operation.



15. Design a practical differentiator that will differentiate signals with frequencies up to 40 kHz . The gain at 10 Hz should be 0.12 . If the op amp used in the design has a unity gain frequency of 2 MHz , what is the upper cutoff frequency of the differentiator?

 
16. In the circuit shown below, the op-amp is ideal and Zener voltage of the diode is 2.5 volts. At the input, unit step voltage is applied, i.e. $v_{IN}(t) = u(t)$ volts. Also, at $t = 0$, the voltage across each of the capacitors is zero. Find the time ' t ' in milliseconds, at which the output voltage v_{OUT} crosses the Zener break down.



17. Using Karnaugh Map solve the given equation to reduce the number of gates used.

$$Y = ABCD + \bar{A}BCD + AB\bar{C}D + ABC\bar{D}$$

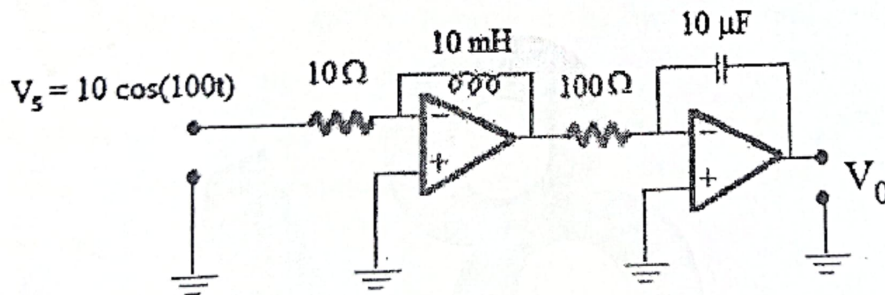8. In the figure given below assume the ideal op amp is used. Find the output voltage if an input signal $V_s = 10 \cos(100t)$ is applied.



- . Draw the logical circuit of an synchronous decade counter.

(4 × 3 = 12 weightage)